

KATHMANDU UNIVERSITY
End Semester Examination c.
November/December, 2023

Marks Scored:

Level : B.E.
Year : II

Course : EEEG 204
Semester : I

Exam Roll No. :

Time: 30 mins.

F. M. : 10

Registration No.:


Date 29 NOV 2023

SECTION "A"

[20 Q. \times 0.5 = 10 marks]

Choose and encircle in the most appropriate option

- When a PN junction diode is reverse biased, _____.
 - electrons and holes are attracted and move towards depletion region.
 - electrons and holes move away from depletion region.
 - width of potential barrier decreases.
 - no changes in potential barrier.
- The knee voltage of Silicon diode is _____.
 - 0.3 V
 - 0.4 V
 - 0.5 V
 - 0.7 V
- In full-wave rectification, if input frequency is 50 Hz then output frequency is _____.
 - 50 Hz.
 - 75 Hz
 - 100 Hz
 - 150 Hz
- A half-wave rectifier has an input voltage of 240 V r.m.s. If the step-down transformer with a turns ratio 8:1 is used, the peak load voltage will be _____.
 - 42.5 V
 - 30 V
 - 86.5 V
 - 240 V
- Rectification efficiency of a half wave rectifier without filter is nearly equal to _____.
 - 81.6 %
 - 71 %
 - 61 %
 - 41 %
- The emitter-base junction of a bipolar transistor is _____.
 - always forward bias
 - always reverse bias
 - open junction
 - neither forward or reverse bias
- In Zener diode, _____.
 - negative resistance characteristics exists
 - forward voltage rating is high.
 - sharp breakdown occurs at a low reverse voltaged.
 - All of the above
- In a transistor, base current is about _____ of the emitter current.
 - 5%
 - 50%
 - 75%
 - 95%
- The element that has the biggest size in a transistor is _____.
 - emitter
 - base
 - collector
 - emitter-base junction

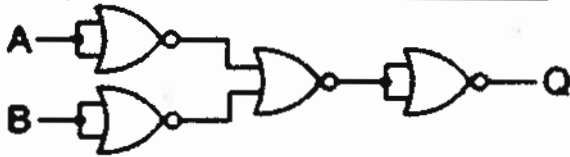10. The total collector current $I_C = \alpha I_E + \underline{\hspace{2cm}}$.
 a. I_{CBO} b. I_{CEO} c. I_B d. βI_B
11. A non-inverting closed loop op amp circuit generally has a gain factor _____
 a. less than one b. equal to one
 c. zero d. greater than one
12. While designing digital to analog converter, _____ circuit is used.
 a. non-inverter b. summer
 c. voltage follower d. differential amplifier
13. Differential amplifiers are used in, _____
 a. instrumentation amplifiers. b. voltage followers
 c. voltage regulators d. buffers
14. The self-generating type transducers are _____ transducers.
 a. secondary b. primary c. passive d. active
15. _____ is one example of digital transducer.
 a. Strain gauge b. Encoder c. Thermistor d. LVDT
16. Air friction damping is used in _____.
 a. moving iron b. moving coil c. induction d. all of the mentioned
17. _____ is not the logic gate.
 a. AND b. NAND c. NOT d. IF
18. In an op-amp, the input impedance is _____ and the output impedance is _____.
 a. high; high b. low; low c. low; high d. high; low
19. The output of the given logic gate is equivalent to _____.


```

graph LR
  A --- NOT1[NOT]
  B --- NOT2[NOT]
  NOT1 --- OR[OR]
  NOT2 --- OR
  OR --- NOT3[NOT]
  NOT3 --- Q
  
```

 a. NOR b. OR c. NAND d. AND
20. There are _____ min-terms for 3 variables (a, b, c).
 a. 8 b. 4 c. 2 d. 0

KATHMANDU UNIVERSITY
End Semester Examination [C]
November/December, 2023

29 NOV 2023

Level : B.E.
Year : II
Time : 2 hrs. 30 mins.

Course : EEG 204
Semester : I
F. M. : 40

SECTION "B"
[5 Q. × 8 = 40 marks]

Attempt *ANY FIVE* questions. Assume suitable data if necessary, Symbol has their usual meaning.

1.

- a. Explain full-wave bridge rectifier circuit and derive its efficiency. [2+2=4]
b. In reference to Figure-1, find the Zener current (I_Z). [4]

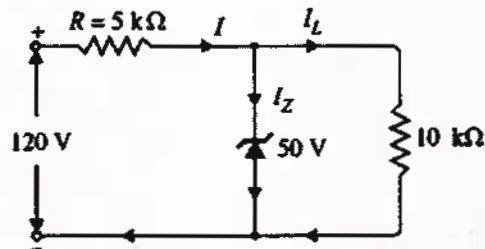


Figure 1

2.

- a. Discuss the working principle of NPN transistor with the help of circuit diagram. [4]
b. In reference to figure 2, draw a load line and determine Q point, if $R_1 = 5.6\text{ k}\Omega$.
(Assume the standard values if necessary) [1+3=4]

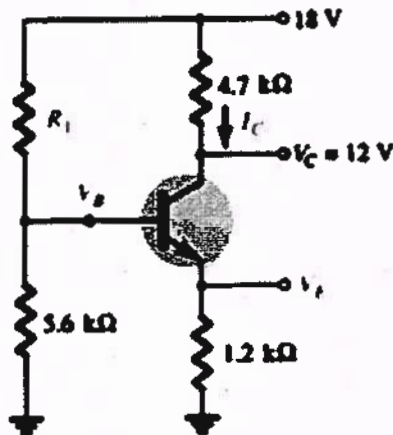


Figure 2

3.

- a. In BJT configurations, what is the meaning of alpha and beta? Also, derive their mathematical relation. [1+3=4]
b. What is op-amp? Derive the gain of non-inverting op-amp. [1+3=4]

4.

- a. Discuss summing amplifier using op-amp. Also derive the expression for three input voltages. [2+2=4]
- b. Discuss D/A conversion with one example. [4]

5.

- a. What are the universal gates? Represent the expression, $F = A + B$ with the help of universal gate. [2+2=4]
- b. Reduce the logic expression, $F = A'B'C + AB'C' + ABC' + ABC$ and draw the logic diagram of reduced expression. [4]

6.

- a. Explain the working principle of permanent magnet moving coil instrument. [4]
- b. Explain data logger with the help of block diagram and write its application. [3+1=4]